

$$\vec{F}_E = \frac{1}{4\pi\epsilon_0} \sum_i \frac{q_i q_z}{r_z^2} \hat{r}_z$$

(전기력) $[\vec{F}_E = N]$

$$\vec{F}_E = \gamma \vec{E}$$

$$[E] = \frac{[F]}{[q]} = \frac{N}{C} = \frac{V}{m}$$

$$\vec{E} = \frac{1}{4\pi\epsilon_0} \sum_i \frac{q_z}{r_z^2} \hat{r}_z$$

(전기장)

$$V = V(A) - V(B)$$

$$= \int_A^B \vec{E} \cdot d\vec{l}$$

$$\vec{E} = -\vec{\nabla} V$$

$$\vec{\nabla} = \frac{\partial}{\partial x} \hat{x} + \frac{\partial}{\partial y} \hat{y} + \frac{\partial}{\partial z} \hat{z}$$

$$E_p = \frac{1}{4\pi\epsilon_0} \sum_i \frac{q_i q_z}{r_z}$$

(전기위치에너지)

$$E_p = \gamma V$$


$$V = \frac{1}{4\pi\epsilon_0} \sum_i \frac{q_z}{r_z}$$

$$[V] = \frac{C}{V} = V(\text{볼트})$$

(전위)

* 전기용량 : $C = \frac{Q}{V}$, $[C] = \frac{C}{V} = F$ (페럿)

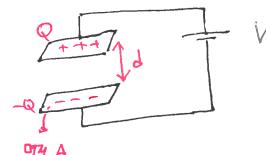
① 평행판 축전기 : $E = \frac{\sigma}{\epsilon_0}$, $C = \epsilon_0 \frac{A}{d}$




$$W = \frac{Q^2}{2C} = \frac{QV}{2} = \frac{CV^2}{2}$$

: 축전기의
저장된
전기에너지

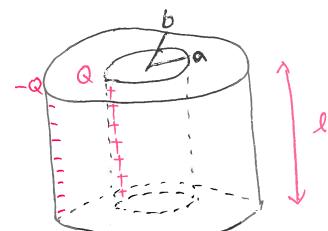② 원통형 축전기 : $E = \frac{Q}{2\pi\epsilon_0 l r}$, $C = \frac{2\pi\epsilon_0 l}{\ln(b/a)}$



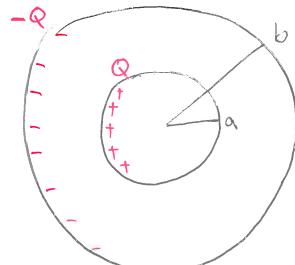③ 구형 축전기 : $E = \frac{i}{4\pi\epsilon_0} \frac{Q}{r^2}$, $C = \frac{4\pi\epsilon_0 ab}{b-a}$



* 전기용량을 구하는 법


$$\Rightarrow \text{Gauss 법칙을 사용하여 } E \text{를 구한다} : \text{인} E = \oint \vec{E} \cdot d\vec{s} = \frac{Q_{in}}{\epsilon_0}$$

$$\Rightarrow V = V(A) - V(B) = \int_A^B \vec{E} \cdot d\vec{l} : E \text{를 대입하여 } V \text{를 구한다}$$

$$\Rightarrow C = \frac{Q}{V} : V \text{를 대입하여 } C \text{를 구한다.}$$

* 등가 전기용량 (C)

① 직렬연결

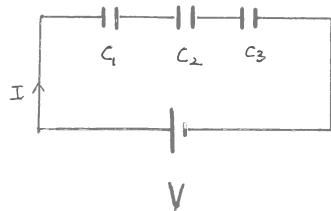


$$V = V_1 + V_2 + V_3 = \left(\frac{1}{c_1} + \frac{1}{c_2} + \frac{1}{c_3} \right) Q$$

$$Q = c_1 V_1 = c_2 V_2 = c_3 V_3$$

$$I = I_1 = I_2 = I_3$$

$$\therefore \text{등가 전기용량 } C = \frac{Q}{V} = \frac{1}{\frac{1}{c_1} + \frac{1}{c_2} + \frac{1}{c_3}}$$

② 병렬 연결

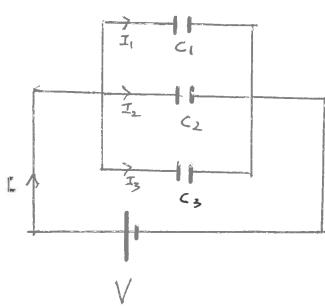

$$V = V_1 = V_2 = V_3$$

$$I = I_1 + I_2 + I_3$$

$$Q = (c_1 + c_2 + c_3) V$$

$$Q_1 = c_1 V_1, \quad Q_2 = c_2 V_2, \quad Q_3 = c_3 V_3$$

$$\therefore \text{등가 전기용량 } C = \frac{Q}{V} = c_1 + c_2 + c_3$$


* 전기용량 : $C = \frac{Q}{V}$

* 축전기에 저장된 전기에너지 : $W = \frac{Q^2}{2C} = \frac{QV}{2} = \frac{CV^2}{2}$

* 전기 에너지 밀도 : $U_E = \frac{\text{전체 전기에너지}}{\text{축전기의 부피}} = \frac{1}{2} \epsilon_0 E^2$

* 등가 저항 (R)

① 직렬 연결

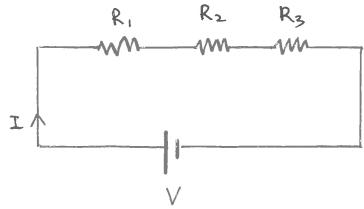


$$I = I_1 = I_2 = I_3$$

$$V = V_1 + V_2 + V_3$$

$$I = \frac{V}{R_{\text{tot}}}$$

$$\therefore R_{\text{tot}} = R_1 + R_2 + R_3 \quad \therefore \text{등가저항}$$

② 병렬 연결

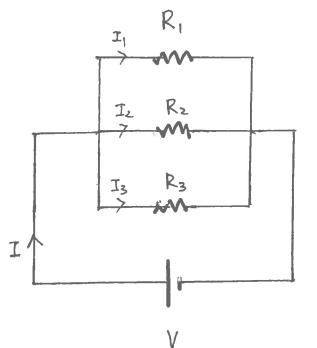

$$V = V_1 = V_2 = V_3$$

$$I = I_1 + I_2 + I_3$$

$$I = \frac{V}{R_{\text{tot}}}$$

$$\therefore R_{\text{tot}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

* 음의 법칙

$$⑨ \boxed{V = IR} , \quad R \equiv \rho \frac{l}{A} = (\text{비저항}) \times \frac{\text{도선의 길이}}{\text{단면적}} \quad \therefore \text{저항.}$$

$$⑩ \boxed{\vec{J} = \sigma \vec{E}} , \quad [\sigma] = \frac{[\vec{J}]}{[\vec{E}]} = \frac{A/m^2}{V/m} = \frac{A}{Vm} = \frac{1}{(V/A)^m} = \frac{1}{\Omega m}$$

$$J = \frac{I}{A} = \frac{\text{전류}}{\text{단면적}} \quad \therefore \text{전류밀도} \quad , \quad [\rho] = \frac{1}{[\sigma]} = \Omega m$$

σ : 전기 전도도 (conductivity)

$$\rho = \frac{1}{\sigma} = \frac{1}{\text{전기전도도}} \quad \therefore \text{비저항 (resistivity)}$$

* 전력 : 단위 시간당 공급하는 에너지

$$P = V I = I^2 R = \frac{V^2}{R} \quad : \text{전력 (Power)}$$

$$[P] = \frac{J}{Sec} = W (\text{와트})$$

$$P = \frac{dW}{dt} = \frac{V d\varphi}{dt} = V \left(\frac{d\varphi}{dt} \right) = V I$$

* 키르히호프 법칙

① 전압법칙 or 폐회로법칙 : $\sum_{\lambda} \Delta V_{\lambda} = 0$

② 전류법칙 or 보기접법칙 : $\sum_{\lambda} I_{\lambda} = 0$